

1. Module details and its structure

Subject Name	Physics
Course Name	Physics (Physics Part 1 Class XII)
Module Name/Title	Unit-02, Module-07: Potentiometer Chapter-03: Current Electricity
Module Id	Leph_10307_eContent
Pre-requisites	Resistance, resistance of a wire, potential drop, electromotive force, Terminal potential difference, ohm's law, internal resistance, ohm's law, Wheatstone bridge, meter bridge, galvanometer
Objectives	<p>After going through this module the learner will be able to:</p> <ul style="list-style-type: none"> • Understand the concept of potential gradient • Know the design of a potentiometer • Compare emf of two primary cells, determine the emf of a cell and determine the internal resistance of a cell using a potentiometer
Keywords	Potentiometer, emf, jockey, internal resistance of a primary cell, comparison of emf of two primary cells .determine the emf of a cell without voltmeter

2. Development Team

Role	Name	Affiliation
National MOOC Coordinator (NMC)	Prof. Amarendra P. Behera	Central Institute of Educational Technology, NCERT, New Delhi
Programme Coordinator	Dr. Mohd Mamur Ali	Central Institute of Educational Technology, NCERT, New Delhi
Course Coordinator / PI	Anuradha Mathur	Central Institute of Educational Technology, NCERT, New Delhi
Subject Matter Expert (SME)	Dinesh Tyagi	Air Force School Hindan, Ghaziabad, U.P.
Review Team	Associate Prof. N.K. Sehgal (Retd.)	Delhi University
	Prof. V. B. Bhatia (Retd.)	Delhi University
	Prof. B. K. Sharma (Retd.)	DESM, NCERT, New Delhi

Table of content

1. Unit Syllabus
2. Module wise break up of unit syllabus
3. Words you must know
4. Introduction
5. Potentiometer
6. Applications of potentiometer
7. Sensitivity of potentiometer
8. Solved examples
9. Problems for practice
10. Summary

1. UNIT SYLLABUS

Electric current, flow of electric charges in a metallic conductor, drift velocity and mobility and their relation with electric current; Ohm's law, electrical resistance, V-I characteristics (linear and non-linear), electrical energy and power, electrical resistivity and conductivity.

Carbon resistors, colour code for carbon resistors, series & parallel combinations of resistors and temperature dependence of resistance

Internal resistance of a cell, Potential difference and emf of a cell, combination of cells in series and in parallel

Kirchhoff's laws and simple applications; Wheatstone bridge and metre bridge

Potentiometer- principle and its application to measure potential difference and for comparing emf of two cells; measurement of internal resistance of a cell

2. MODULE WISE DISTRIBUTION OF UNIT SYLLABUS 8 MODULES

The above unit has been divided into 8 modules for better understanding.

Module 1	<ul style="list-style-type: none"> • Electric current, • Solids liquids and gases • Need for charge carriers speed of charge carriers in a metallic conductor • flow of electric charges in a metallic conductor • drift velocity, • mobility and their relation with electric current • Ohm's law,
Module 2	<ul style="list-style-type: none"> • Electrical resistance, • V-I characteristics (linear and non-linear), • Electrical energy and power, • Electrical resistivity and conductivity • Temperature dependence of resistance
Module 3	<ul style="list-style-type: none"> • . Carbon resistors, • Colour code for carbon resistors; • Metallic Wire resistances • Series and parallel combinations of resistors • Grouping of resistances • Current and potential differences in series and parallel circuits
Module 4	<ul style="list-style-type: none"> • Internal resistance of a cell, • Potential difference and emf of a cell, • Combination of cells in series and in parallel.

	<ul style="list-style-type: none"> • Need for combination of cells
Module 5	<ul style="list-style-type: none"> • Kirchhoff's Rules • Simple applications. of Kirchhoff's Rules for calculating current s and voltages <p>Numerical</p>
Module 6	<ul style="list-style-type: none"> • Wheat stone bridge • Balanced Wheatstone bridge condition derivation using Kirchhoff's Rules • Wheatstone bridge and Metre Bridge. • Application of meter bridge
Module 7	<ul style="list-style-type: none"> • Potentiometer – • Principle • Applications to • Measure potential difference • Comparing emf of two cells; • Measurement of internal resistance of a cell. <p>Numerical</p>
Module 8	<ul style="list-style-type: none"> • Numerical • Electrical energy and power

Module 7

3. WORDS YOU MUST KNOW

- **Chemical cell:** An assembly of electrolyte and electrodes which convert chemical energy into electrical energy example simple voltaic cell, Daniel cell, Leclanche cell, dry cell.

- **Ohms law:** The potential difference across a metallic wire is directly proportional to the current passing through it, provided the temperature and physical conditions of the metallic wire remain the same. Metals that follow ohms law over a large range of temperature variation are called ohmic resistances. Electrolytes, semiconductor materials are no ohmic , means do not obey ohm's law: $V=IR$
- **Resistance:** the obstruction offered by a conducting wire to current whenever a potential difference is applied across it.
- **Potential drop across resistance:** It is the potential difference between ends of a resistance. In Ohm's law $V = IR$ where, V is potential drop across resistance (for details see role of resistance in module 1).
- **Electromotive Force (EMF):** It is the force which makes change to flow in an electrical circuit. It is defined as Work done in moving a unit positive charge once in a closed circuit.
- **EMF of a cell (ϵ):** It is the max. Potential difference between electrodes of a cell when no current being drawn from cell.
- **TPD of a cell (V):** It is the max. Potential difference between electrodes of a cell when current is being drawn.
- **Internal resistance of a cell (r):** It is the resistance offered by electrolyte to current flowing.
- **Galvanometer:** It is the device which detects small current. A galvanometer can indicate the direction of current and also indicate relative magnitude of current in a circuit or a branch of a circuit.
- **Jockey:** It is a metallic rod whose one end has a knife edge which slides over the wire and other end is connected.

4. INTRODUCTION

In our previous module we have studied basic electrical circuits; the motivation for our study is to recognize series parallel connection of resistances and cells. The cells have internal resistance on account of the electrolyte and the chemicals .The application of basic knowledge to design useful circuits, demands thorough and vast knowledge of each of the quantities. We

are learning in steps the idea of distribution of currents, as we did using Kirchhoff's rules. We learnt a method of finding the value of an unknown resistance using a meter bridge. The principle of Meter Bridge is Wheatstone bridge and the condition for balanced Wheatstone bridge allows us the simple calculation of resistance of a wire.


In this module we will learn the principle and application of potentiometer.

Think about this, suppose we are given a cell and we wish to know its emf or internal resistance, how shall we measure it?

We need a potentiometer to find an emf or internal resistance of a given cell.

We know that resistance is obstruction in path of flow of current.

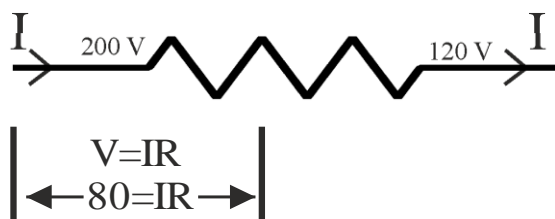From ohms law **we can find the** electric resistance, if our problem is according to the See fig.



The incoming side has say a potential 200 V and outgoing end has potential 120 V .

- ⊗ There is a potential drop of 80 V . In Ohm's law ($V=IR$), V is potential difference between two ends of resistance, hence $80=IR$.
- ⊗ For this reason we always say “potential drop across resistance”.
- ⊗ A voltmeter connected across R will measure 80 V

ELECTROMOTIVE FORCE (emf) (E)

It is the force which derives the charge in a closed path.

Sources of EMF are:- Cell ,generators ,Dynamo

Q: Why do we need a cell in a circuit?

A: Charge can move on its own from higher to lower potential but cannot go on its own from lower to higher potential. So, to run charge in a closed path, we need a source EMF- a cell.

- ⊗ **Don't get confused that emf is force. EMF is not a force but is work done in moving a unit positive charge once in a closed path.**
- ⊗ **EMF of a cell is defined as the maximum potential difference between the terminals of the cell when no current is being drawn from the cell.**

TERMINAL POTENTIAL DIFFERENCE OF A CELL (TPD) 'V'

It is defined as maximum potential difference between the terminals of a cell when current is being drawn from the cell.

The basic difference between emf and TPD of cell is that in emf no current is being drawn from the cell but in TPD current is being drawn from the cell.


INTERNAL RESISTANCE OF A CELL: (r)

It is the resistance offered by the electrodes and electrolytes of the cell to the current flowing.

The value of internal resistance depends upon:-

- a) Nature of electrodes
- b) Nature of electrolyte
- c) Concentration of electrolyte
- d) Distance between electrodes ($d \propto r$)
- e) Area of electrodes emerged in the electrolyte
 - a. Increase area emerged, decrease in internal resistance for this reason, we pour water in cars or inverter batteries.
- f) Temperature of electrolyte:- Inversely proportional

RELATION BETWEEN EMF (E) AND TPD (V)

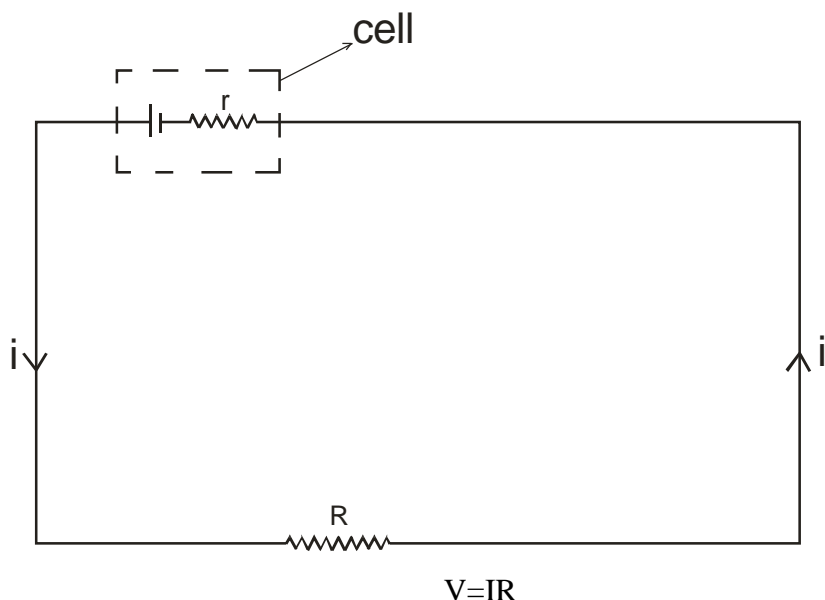

By applying Kirchhoff's Voltage rule

$$-IR - Ir + E = 0$$

$$-V - Ir + E = 0$$

$V = E - Ir$ for discharging of cell

$E > V$

The above equation is for discharging of cell. Note that in discharging of cell emf > TPD

Equation for charging of cell is given by:

$$V = E + Ir$$

$V > E$ for charging of cell

For charging of cell TPD > emf

Expression for internal resistance(r) of cell

From $V = E - Ir$

$$Ir = E - V$$


$$r = \left(\frac{E - V}{I} \right) R$$


5. POTENTIOMETER

It is an electrical device used to measure accurately emf of a cell or potential difference between two points on an electrical circuit.

Typical potentiometer

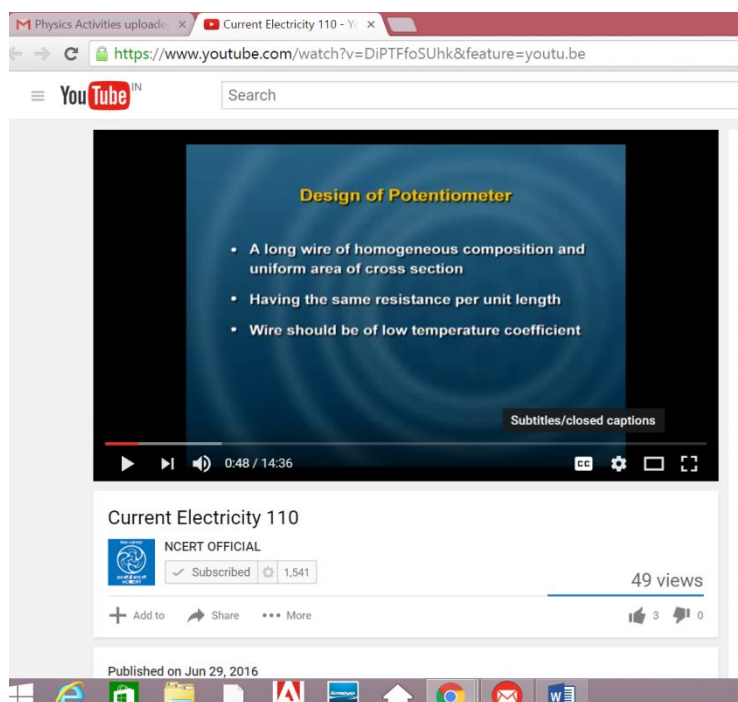Watch <https://www.youtube.com/watch?v=DiPTFfoSUhk&feature=youtu.be>



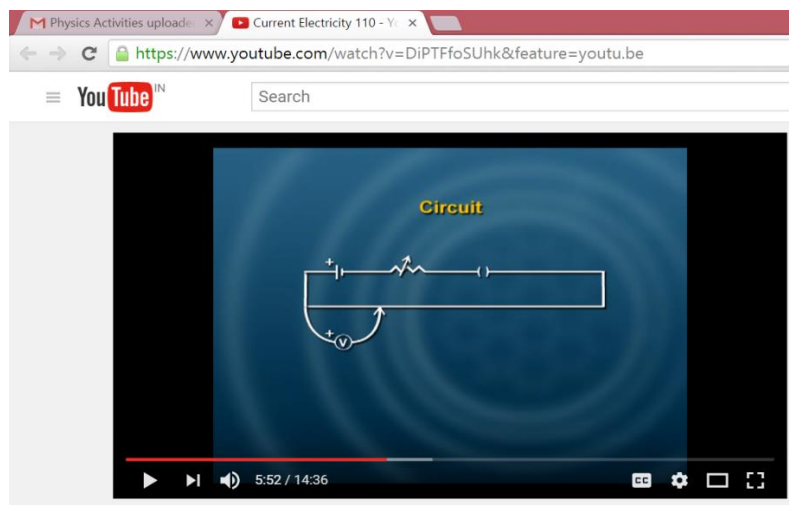

Simplified potentiometer

Working principle

Based on the fact that potential drop across a wire is directly proportional to length of that portion, provided area of cross-section and current through the wire remains constant.

We know $V = IR$

$$R = \rho \frac{l}{A}$$

$$V = I \rho \frac{l}{A} \quad \left(\frac{I\rho}{A} \text{ is constant}\right)$$

$$V \propto l$$

$$V = k l \text{ Where, } k = \frac{I\rho}{A};$$

Potential drop per unit length

- $k = \frac{V}{l}$ is called potential gradient. It is defined as potential drop per unit length of potentiometer wire. Its S.I. unit is volt per meter (Vm^{-1}).

- As k gives potential drop of a unit length of wire. To find potential drop of any length of potentiometer wire, simply multiply that length with k .
- Your NCERT book has the potentiometer diagram as shown this is a schematic representation of a six wire potentiometer,
which would mean a length of wire = $6 \times 100 \text{ cm} = 600 \text{ cm}$
as we said the length of the wire can be chosen for required need of potential drop per cm of potentiometer wire

EXAMPLE:

Let potential drop per cm is say 0.02 V cm^{-1} . Therefore $k = 0.02 \text{ V cm}^{-1}$. If we wish to find potential drop of 30 cm length, then

$$V = k l$$

$$V = 0.02 \times 30 \text{ V} = 0.02 \frac{\text{V}}{\text{cm}} \times 30 \text{ cm}$$

$$V = 0.6 \text{ V}$$

To explain the Principle of potentiometer


A current I flows through the wire which can be varied by a variable resistance (rheostat, R) in the circuit. Since the wire is uniform, the potential difference between A and any point at a distance l from A is $V = k (l)$ where k as we have said is the potential drop per unit length.

6. APPLICATIONS OF POTENTIOMETER**a) To find emf of a cell.****Apparatus required and Circuit connections****You will need:**

- A potentiometer

- A galvanometer
- A resistance box
- A driver cell to create a potential difference across the length of the wire which should be greater than the expected emf of the cell
- Connecting wire

Circuit diagram:

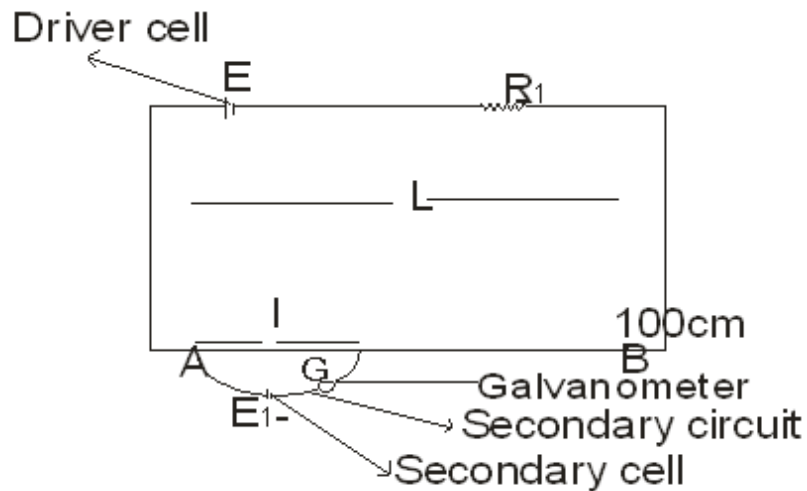

AB is the potentiometer wire; connect the driver cell across it, using suitable resistance from the resistance box

Next connect the positive of the test cell to the terminal connected to the positive of the driver cell .connect the other terminal of the test cell to the jockey

- At the balance length l galvanometer shows no deflection means there is no current being drawn from secondary cell E_1 . Therefore balance length corresponds to emf.

$$E_1 = kl$$



b) To compare emf of two cells

Watch <https://www.youtube.com/watch?v=fguE3Pg54dE&feature=youtu.be>

Apparatus you will need

- Potentiometer
- Driver cell E
- Galvanometer G
- The two test cells E_1, E_2
- keys and connecting wires

Circuit connections

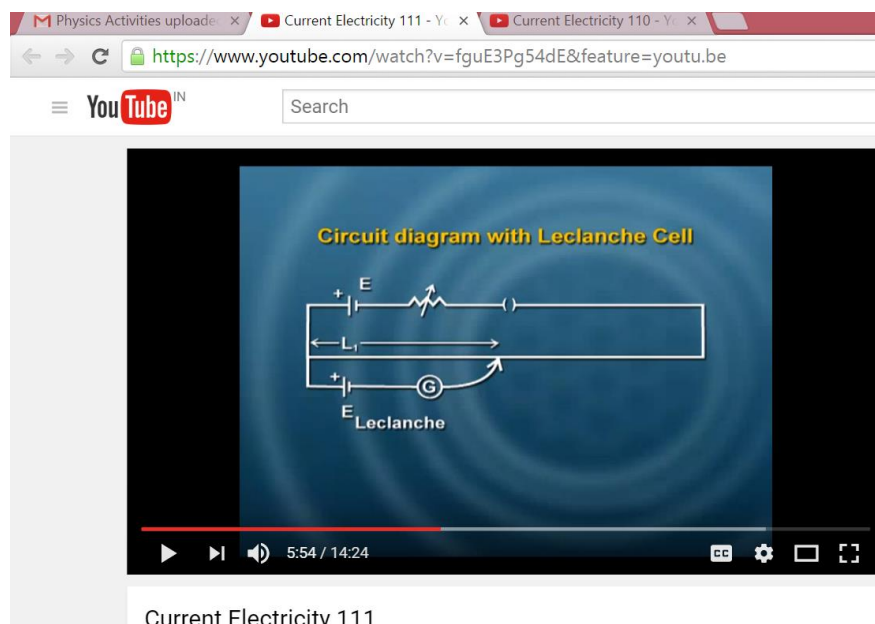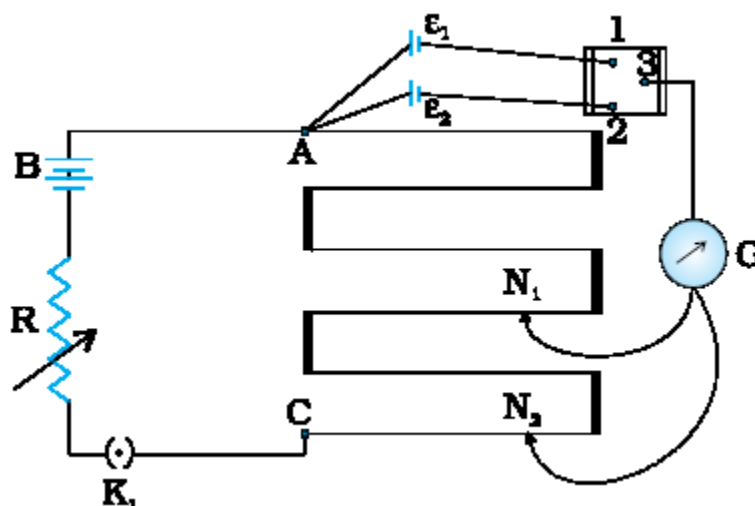

Schematic diagram can be given as:

- When key K_1 is closed and K_2 open, balancing length l_1 corresponds to emf E_1 .

$$E_1 = k l_1$$

- When key K_2 is closed and K_1 open, balancing length l_2 corresponds to emf E_2 .

$$E_2 = k l_2$$

$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$

Watch Check out the graph between l_2 vs l_1

The screenshot shows a YouTube video player with the following content:

- Browser tabs: Physics Activities upload..., Current Electricity 111 - Y..., Current Electricity 110 - Y...
- Address bar: <https://www.youtube.com/watch?v=fguE3Pg54dE&feature=youtu.be>
- YouTube logo and search bar.
- Video player showing a graph titled "Graph of L_2 v/s L_1 ".
- Equation: $E_1 L_2 = E_2 L_1$
- Graph axes: y-axis is L_2 , x-axis is L_1 .
- A slope triangle is drawn with the slope labeled m .
- Equation: $L_2 = \frac{E_2}{E_1} L_1$
- Video player controls: play, volume, 12:59 / 14:24, CC, settings, full screen.
- Video title: Current Electricity 111


b) To find internal resistance of a cell

Watch <https://www.youtube.com/watch?v=CuDuFqdiFoM&feature=youtu.be>


Apparatus used

- Driver cell
- Potentiometer
- Test cell
- Resistance box
- Galvanometer
- Jockey
- Connecting wires and keys

Circuit diagram:

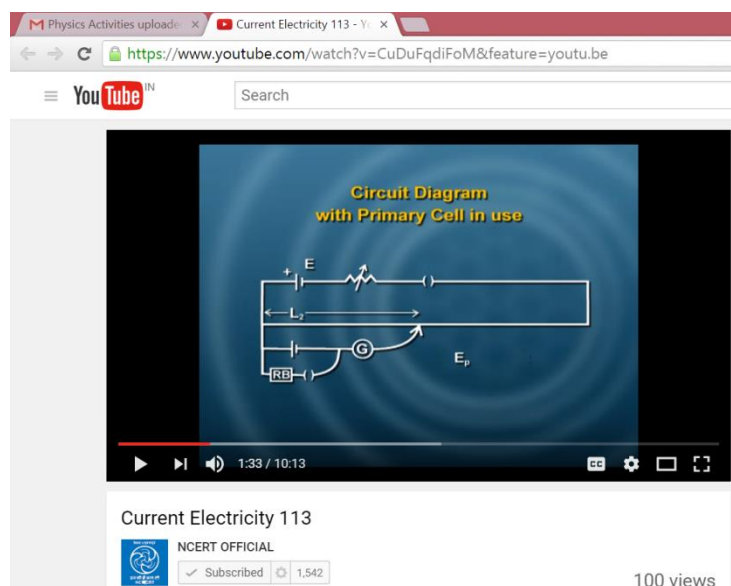

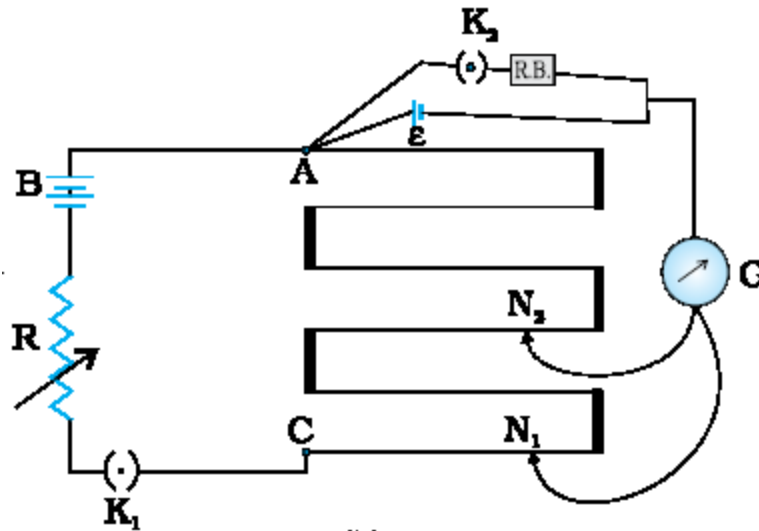So if our balancing length when galvanometer shows zero deflection is l_1 without resistance R in the circuit or when the circuit is open.



When key k_1 is open balancing length l_1 at N_1 gives emf E_1 .

$$E_1 = k l_1$$

- When key k_1 is closed current is being drawn from cell E_1 therefore balancing length l_2 at N_2 gives TPD(V) of cell E_1 .
- Therefore $V = k l_2$

$$\frac{E_1}{V} = \frac{l_1}{l_2}$$

- *Expression* for internal resistance (r) is

$$r = \left(\frac{E_1 - V}{V} \right) R$$


$$= \left(\frac{E_1}{V} - 1 \right) R$$

$$r = \left(\frac{l_1}{l_2} - 1 \right) R$$


IMPORTANT POINTS

- **Current in potentiometer is due to driver cell only. And current in secondary circuit is due to secondary cell only.**

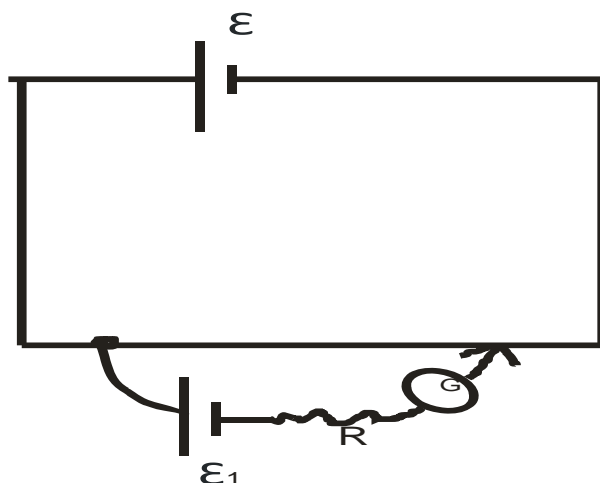- Emf of driver cell should be greater than emf of secondary cell; otherwise we won't get balance point on the potentiometer.
- A resistance in series with secondary cell does not affect the balance point because at balance length no current is drawn from the secondary cell. Hence no potential drop in the resistor.



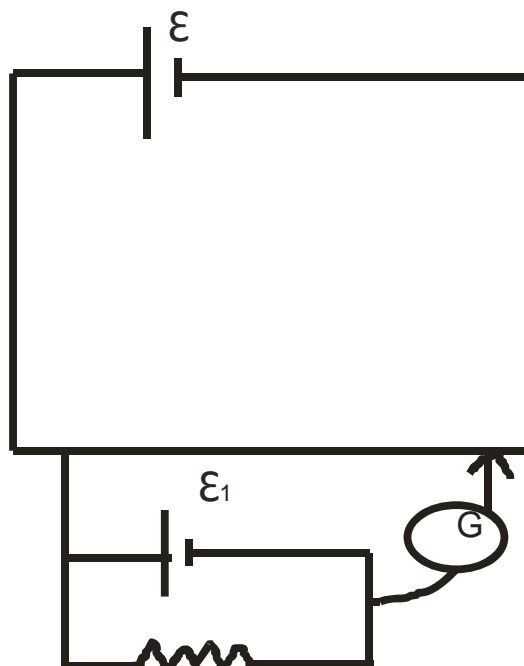- A resistance in parallel to secondary cell affects the balance point because it draws current from the secondary cell.



- If galvanometer shows deflection in one direction, following may be the reason:

- (i) Emf of secondary cell may be greater than emf of primary cell.
- (ii) Connections of secondary cell may be losing.

- Positive ends of both cells, driver cell and secondary cell, should be connected at zero end of the potentiometer.
- Potentiometer is preferred over voltmeter because potentiometer draws no current from the cell, emf of which is being measured. Thus potentiometer is an ideal voltmeter.

What if your lab does not have a potentiometer?

- Take a wooden strip
- Put a resistance wire tight between the ends using a suitable nail.
- You will need a scale and a galvanometer
- You can use dry cells as driver cells. you can find out whether a particular cell is in discharged condition or not

7. SENSITIVITY OF POTENTIOMETER

A potentiometer is said to be sensitive if a small potential drop occurs in larger length.

$$V \propto l$$

$$l = \frac{V}{k}$$

For a given potential, l will be large if k (potential gradient) is small.


For potentiometer to be sensitive its k has to be small, which can be done by:

- (i) Increasing length of potentiometer wire since $k = \frac{V}{l}$
- (ii) Decreasing current in the potentiometer since $k = \frac{\rho I}{A}$

8. SOLVED EXAMPLES

EXAMPLE:

Resistance of $R \Omega$ is powered from a potentiometer of resistance $R_0 \Omega$. A voltage V is supplied to the potentiometer. Derive an expression of the voltage fed into the circuit when the slide is in the middle of potentiometer.

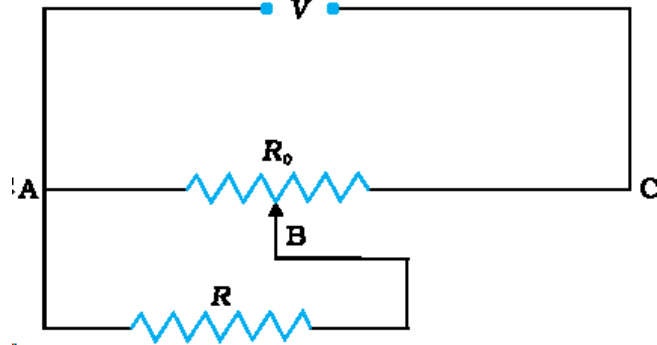**SOLUTION:**

When slide is in the middle of the potentiometer wire, only half of the resistance of potentiometer ($=R_0$) will be between the points A and B. Hence effective resistances (R_1) between A and B is:

$$\frac{1}{R_1} = \frac{1}{R} + \frac{1}{R_0/2}$$

or

$$R_1 = \frac{R_0 R}{R_0 + 2R}$$

Total resistance between A and C = $R_1 + \frac{R_0}{2}$

Current through the potentiometer wire will be


$$I = \frac{V}{R_1 + R_0/2} = \frac{2V}{2R_1 + R_0}$$

The voltage V_1 taken from the potentiometer will be the product of current I and resistance R_1 i.e.

$$V_1 = IR_1 = \frac{2V}{2\left(\frac{R_0R}{R_0+R}\right)+R_0} \times \frac{R_0R}{R_0+2R} = \frac{2VR}{2R+R_0+2R} = \frac{2VR}{R_0+4R}$$

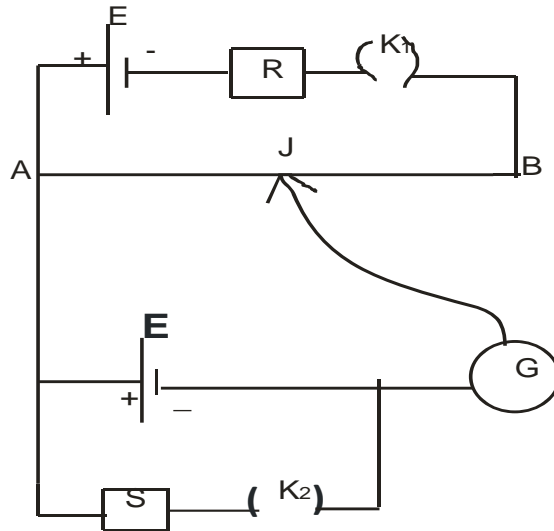EXAMPLE:

Two students X and Y perform an experiment on potentiometer separately using the circuit given below.



Keeping other parameters unchanged, how will the position of null point be affected if

- (i) X increases the value of resistance R in the setup by keeping the key K₁ closed and the key K₂ open
- (ii) Y decreases the value of resistance S in the setup, while the key K₂ remains open and the key K₁ closed.

SOLUTION:

- (i) Current through potentiometer wire decreases. Thus, potential gradient decreases. As $K = \frac{V}{l}$ with the decrease in potential gradient balancing length increases i.e. null point will shift towards 'B'.

- (ii) Current through potentiometer wire remains same i.e. potential gradient does not change.
As a result null point remains same.

EXAMPLE:

In a potentiometer arrangement, a cell of emf 1.25 volts gives a balance point at 35 cm length of the wire. If the cell is replaced by another cell and balance point shifts to 63 cm, what is the emf of the second cell?


SOLUTION:

$$\frac{E_2}{E_1} = \frac{l_2}{l_1}$$

$$E_2 = \frac{63}{35} \times 1.25 = 2.25 \text{ volt}$$

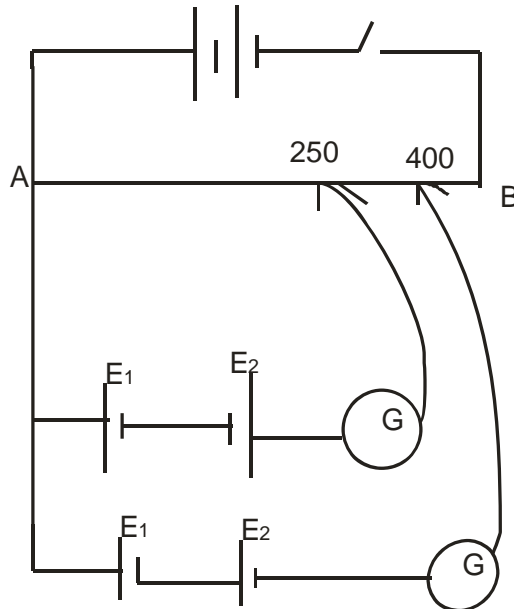EXAMPLE:

Two primary cells of emf E_1 and E_2 ($E_1 > E_2$) are connected to the potentiometer wire AB as shown in the figure. The balancing lengths for the two combinations of the cells are 250 cm and 400 cm, find the ratio of E_1 and E_2 .



SOLUTION:

$$E_1 + E_2 = k(400)$$

$$E_1 - E_2 = k(250)$$


$$\frac{E_1 + E_2}{E_1 - E_2} = \frac{400}{250}$$

On solving we get,


$$\frac{E_1}{E_2} = \frac{13}{5}$$

9. PROBLEMS FOR PRACTICE

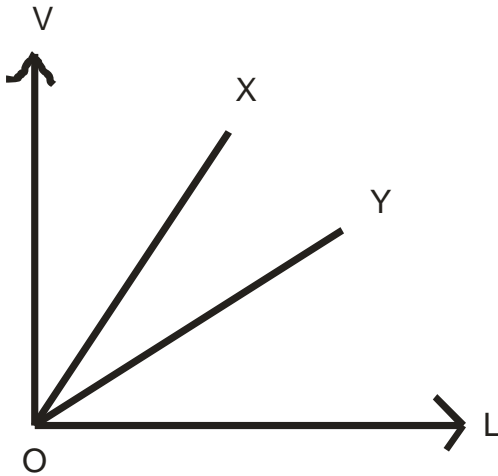
- (i) State the principle of potentiometer. With the help of circuit diagram describe a method to find the internal resistance of a primary cell.
- (ii) What is a potentiometer? Explain its principle of working. How can you compare the emf of two cells using potentiometer?
- (iii) What is Potential gradient? How is it measured? Explain.
- (iv) Can you express the Potential gradient in terms of specific resistance of the wire? If yes, find the relation.
- (v) If the emf of the driving cell be decreased, what will be effect on the position of zero deflection in a potentiometer? Explain.
- (vi) A standard cell of emf 1.08V is balanced by the potential difference across 91cm of a metre long wire supplied by a cell of emf 2V through a series resistor of resistance 2Ω. The internal resistance of the cell is zero. Find the resistance per unit length of the potentiometer wire.
- (vii) The variation of potential difference V with length l in case of two potentiometers X and Y is as shown in the figure. Which one of these two will you prefer for comparing emfs of the two cells and why?



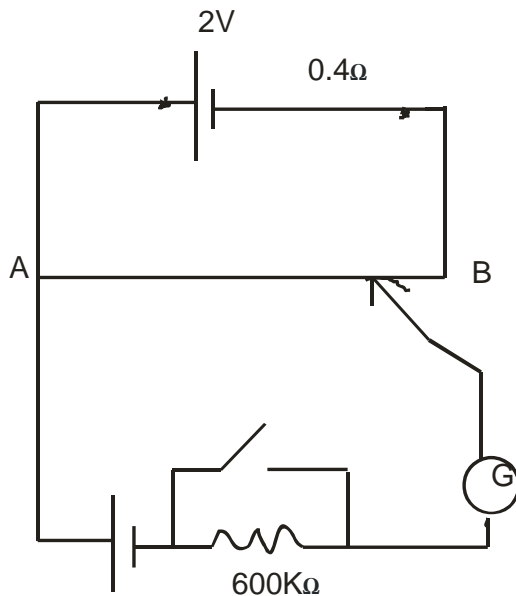
- (viii) In a potentiometer arrangement, a cell of emf 1.25V gives a balance point at 35cm length of the wire. If the cell is replaced by another cell and the balance point shifts to 63cm, what is the emf of the second cell?
- (ix) Figure below shows a potentiometer with a cell of 2.0V and internal resistance 0.40Ω maintaining a potential drop across the resistor wire AB. A standard cell which maintains a constant emf of 1.02V (for very moderate currents upto a few mA) gives a balance point at 67.3cm length of the wire. To ensure very low currents drawn from the standard cell, a very high resistance of $600K\Omega$ is put in series with it, which is shorted close to the balance point. The standard cell is then replaced by a cell of unknown emf ε and the balance point found similarly, turns out to be at 82.3 cm length of the wire.



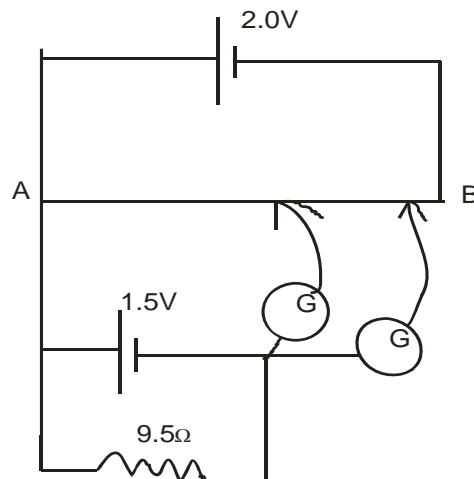- (a) What is the value of ε ?
- (b) What purpose does the high resistance of $600\text{k}\Omega$ have?
- (c) Is the balance point affected by the internal resistance of the driver cell?
- (d) Is the balance point affected by this high resistance?
- (x) Figure shows a 2.0V potentiometer used for the determination of internal resistance of a 1.5V cell. The balance point of the cell in open circuit is 76.3cm . When a resistor of $9.5\ \Omega$ is used in the external circuit of the cell, the balance point shifts to 64.8cm length of the potentiometer wire. Determine the internal resistance of the cell.



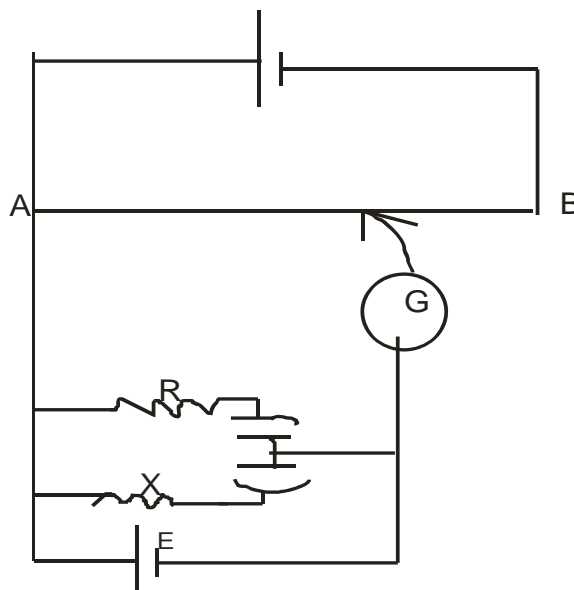- (xi) Figure shows a potentiometer circuit for comparison of two resistances. The balance point with a standard resistor $R = 10.0\Omega$ is found to be 58.3cm, while that with the unknown resistance X is 68.5cm. Determine the value of X . What might you do if you failed to find a balance point with the given cell of emf ϵ ?



- (xii) If the length of the wire be (i) doubled and (ii) halved, what will be effect on the position of zero deflection in a potentiometer? Explain.
- (xiii) Sometimes balance point may not be obtained on the potentiometer wire. Why?
- (xiv) What does the no deflection position in the galvanometer of potentiometer experiment tell us about the flow of current?
- (xv) Why do we prefer a potentiometer to measure emf of a cell rather than a voltmeter?
- (xvi) What do you understand by sensitiveness of a potentiometer and how can you increase the sensitiveness of a potentiometer?
- (xvii) Suggest a method, so that one can use the potentiometer to get a small potential difference say 0.4V for a circuit when the available cells are 1.5 V, 9 V etc

10. SUMMARY

In this module you have learnt:

- Principle of potentiometer
- Applications of potentiometer for
 - ✓ Finding emf of a cell,
 - ✓ Comparing emf of two cells,
 - ✓ Finding the internal resistance of a cell
- Potentiometer sensitivity